

Question:(CSE Batch)

Design a circuit for 4 bit universal shift register controlled by a 2 bit control input and performs the following required operation.

Input		Operation
A	B	
1	1	Parallel Loading
1	0	Left shift
0	1	Right shift