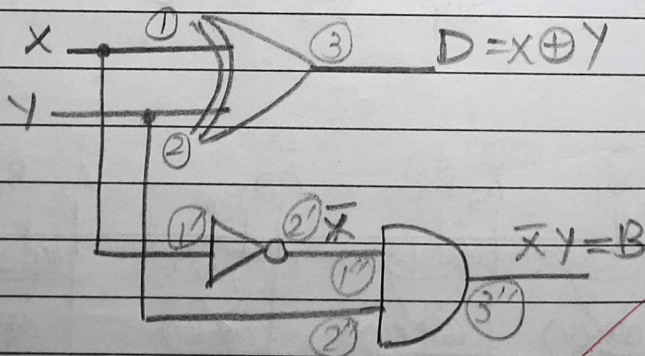


Half-subtractor (≥ 2 input gates)

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = \bar{X}Y + X\bar{Y} = X \text{ XOR } Y = X \oplus Y$$


$$B = \bar{X}Y$$



(1 XOR gate
1 NOT gate
1 AND gate)


✓
Sanyukta
14/1/22

Adder/Subtractor using Full Adder

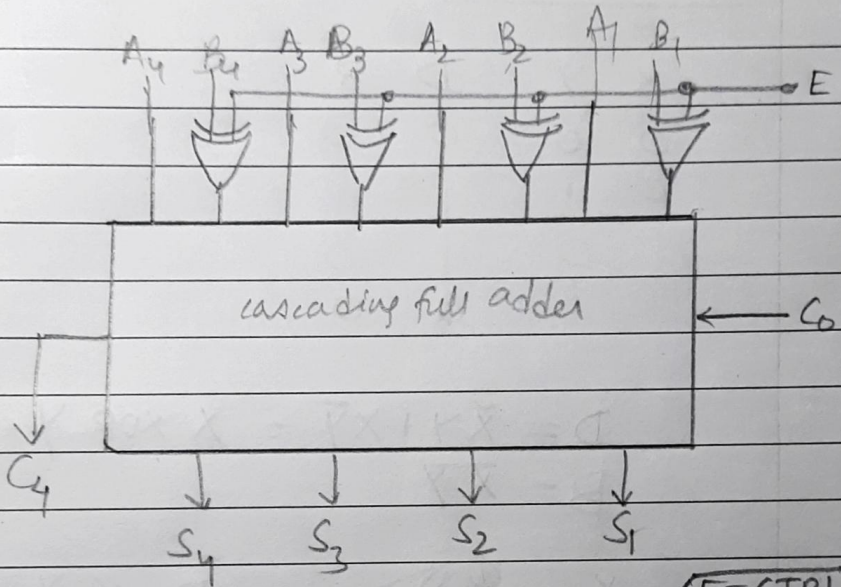

(E=CTRL)

E=0 Adder
E=1 Subtractor by 2's Compl.

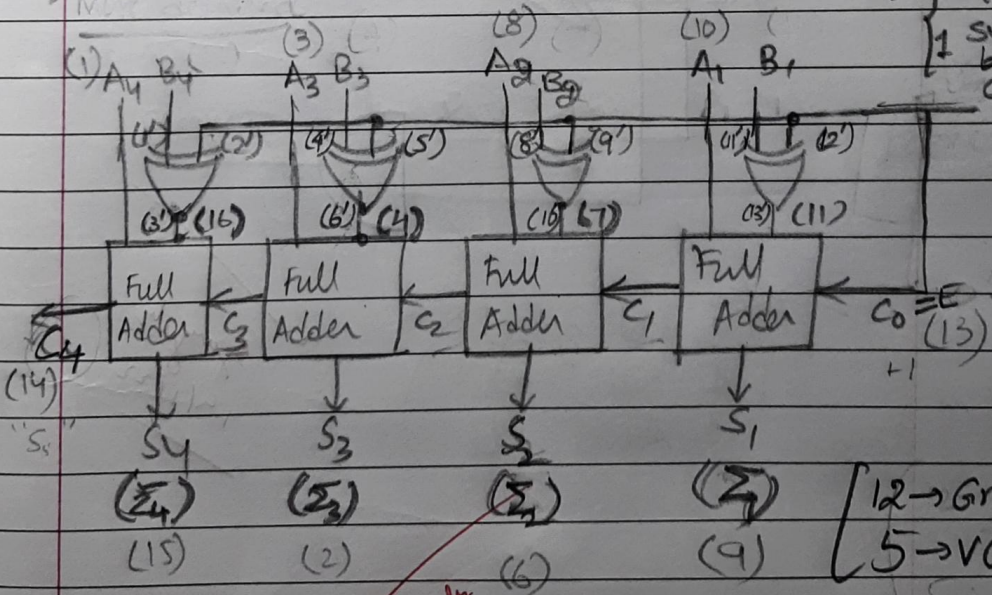

Anguly

14/11/22

$$A + 2's \text{ compl}(B) = A - B$$