

# EE 214: Digital Circuits Laboratory

## LAB - 5

Roll No.: 200010003

- **Aim:** Design and Implementation of *Half-Subtractor* circuit using logic gates, and *4-bit Adder-Subtractor* circuit using a full adder.
- **Summary of the experiment:**
  1. Creation of truth table for Half-Subtractor, and obtaining boolean expressions for Difference (D) and Borrow (B).
  2. Design and Implementation of the Half-Subtractor using XOR, NOT, and AND gates.
  3. Design and Implementation of a 4-bit Adder/Subtractor circuit (that uses 2's complement method) using a full adder.
- **Problem Statement:**
  1. Design and implement a Half-Subtractor circuit using a minimum number of 2-input gates.
  2. Familiarize 74LS83 IC and implement a controlled 4-bit Adder/Subtractor circuit which is controlled by signal CTRL using 74LS83 and minimum number of 2-input gates. (CTRL: 0 for Addition and 1 for Subtraction)
- **Components used:** IC 7408, 7404, 7486, 7483, 1 kilo-ohm resistor array, DIP switches, LED displays, breadboard, power supply.
- **Design Procedure, Circuit Diagrams and Snapshots:**

(attached below)

- **Results and Discussions:**

1. We constructed a truth table for a Half-Subtractor. Then, we derived the boolean expression for it, and implemented it using the AND, NOT, and XOR logic gates. The outputs obtained were Difference (D) and Borrow (B).
2. We modified a full-adder into a 4-bit Adder-Subtractor circuit by adding XOR gates at B-inputs, and keeping a CTRL that controls whether the adder obtains B, or 2's complement of B. Keeping  $C_0 = \text{CTRL}$  ensures that for CTRL = 1, we add 1 to the 1's complement of B, hence obtaining its 2's complement. Also, when CTRL = 0, it makes the XOR gates behave as buffers, and simply allows B to pass.
3. Subtraction of B from A is the same as adding A to the 2's complement of B. We kept this in mind during the design.

- **Conclusion:**

We designed and implemented a Half-Subtractor circuit using the basic/special logic gates (AND, NOT, XOR), and verified the outputs obtained using the truth table. We also implemented a 4-bit Adder/Subtractor circuit using IC 7483 (Full Adder), and utilized 2's complement method with the help of XOR gates.


# Design Procedure and Circuit Diagram

Half-subtractor ( $\geq 2$  input gates)

X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = \bar{X}Y + X\bar{Y} = X \text{ XOR } Y = X \oplus Y$$


$$B = \bar{X}Y$$

 

(1 XOR gate  
1 NOT gate  
1 AND gate)


✓  
Sanyukta  
14/11/22

# Adder/Subtractor using Full Adder

 

(E=CTRL)

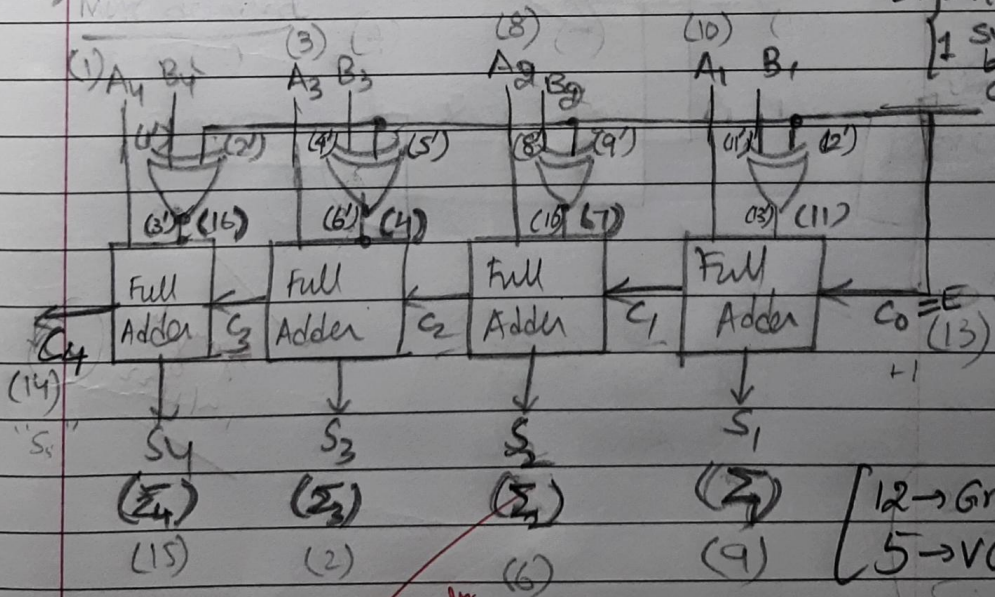$E=0$  Adder  
 $E=1$  Subtractor by 2's Compl.





$12 \rightarrow \text{Gnd}$   
 $5 \rightarrow \text{VCC}$

$$A + 2's \text{ compl}(B) = A - B$$





## Circuit Snapshots

### Problem 1 : Half-Subtractor

  




  




## Problem 2

 

 
$$1110 + 1001 \rightarrow C_4 = 1, S = 0111$$




$$1110 - 1001 \rightarrow C_4 = 1, S = 0101$$



Extra Examples :

 
 
$$0000 + 0001 \rightarrow C_4 = 0, S = 0001$$



$$0001 - 0001 \rightarrow C_4 = 1, S = 0000$$