

Lab-6

→ Design Procedure, Truth Table, and logic diagram

Given Variables: HS(headlights), D(door), IS(ignition), A(Alarm)
 [CLOSED/OFF=0, OPEN/ON=1]

Based on conditions given for alarm ON:-
 condition 1: $HS \cdot IS$
 condition 2: $D \cdot IS$
 $\Rightarrow A = HS \cdot IS + D \cdot IS$

Truth table : (Enable=1) for the negative logic 3-to-8 decoder,

D	IS	HS	A
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$Y_0 = D + IS + HS$$

$$Y_1 = D + IS + \overline{HS}$$

$$Y_2 = D + IS + HS$$

$$Y_3 = D + \overline{IS} + \overline{HS}$$

$$Y_4 = \overline{D} + IS + HS$$


$$Y_5 = \overline{D} + IS + \overline{HS}$$

$$Y_6 = \overline{D} + \overline{IS} + HS$$


$$Y_7 = \overline{D} + \overline{IS} + \overline{HS}$$

Using a 3:8 decoder,
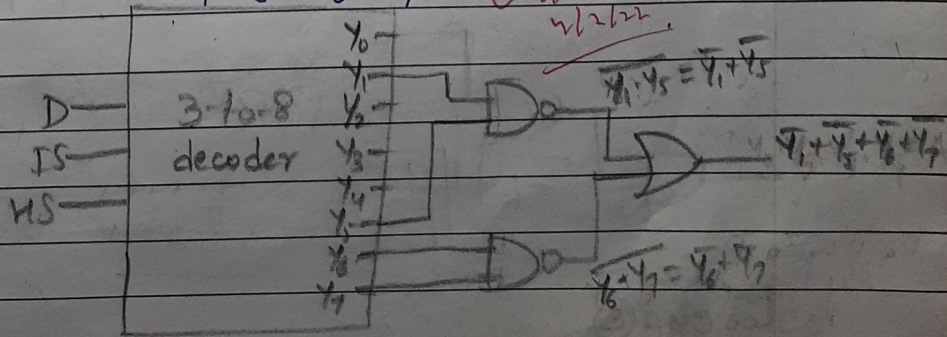
$$A = \overline{Y_1} + \overline{Y_5} + \overline{Y_6} + \overline{Y_7}$$



- using only 2-input NAND gates:

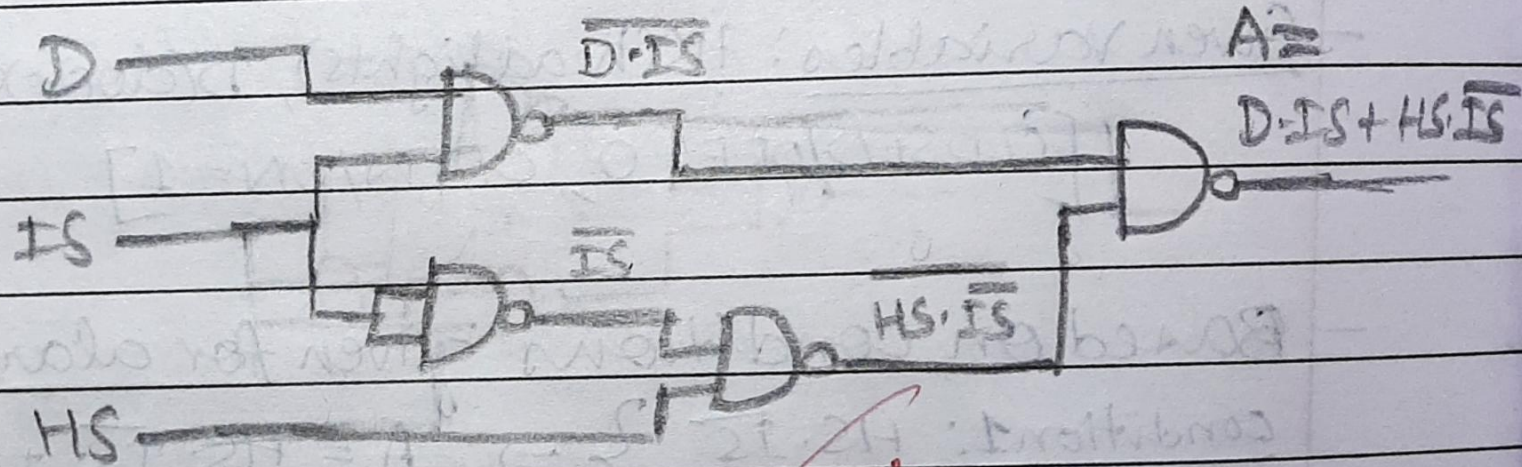

✓
Sengul
22/2/22