

# Introduction to VHDL Programming & Basics of CPLD



॥ सा विद्या या विमुक्तये ॥

ಭಾರತೀಯ ತಂತ್ರ ಜ್ಞಾನ ಸಂಸ್ಥೆ ಧಾರವಾಡ  
भारतीय प्रौद्योगिकी संस्थान धारवाड  
Indian Institute of Technology Dharwad

Presented by  
Mayur Shivamurthy  
Research Scholar  
Dept. of EE , IIT Dharwad

# Hardware Description Language

## *What is the need for HDL?*

- Advances in IC technology have enabled manufactures to develop complex digital electronic circuits.
- Complex digital circuit designs require more time for development, synthesis, simulation and debugging
- HDL solve the problem by allowing hardware software co-design and model the complex circuit at subsystem levels.
- A **synthesizable** HDL code results to an equivalent hardware.
- It is found to be an excellent language for different programmable devices like FPGAs and CPLDs.

# Hardware Description Language

How it is different from C and other programming languages?

<b>HDL</b>	<b>C</b>
Can handle sequential and concurrent instructions	Can handle only sequential instructions
Knowledge of the hardware circuits	written with pure logical or algorithmic thinking.
Limited memory and other logic elements in programmable devices must be taken into account	Resource usages are not critical


# Classification of HDL

VHDL (VHSIC-HDL)	Verilog
It is strongly typed	It is weakly typed
High verbosity	Low verbosity
Case insensitive	Case sensitive
Non C like	More C like
Upto gate level implementation only	Transistor level implementation is possible

# Features of VHDL

- Supports concurrent and sequential execution of statements.
- It possesses IEEE standards.
- Like C, VHDL also supports different data types, conditional, relational, logical, arithmetic operators.
- Supports 3 different modelling styles
  1. Dataflow
  2. Behavioural
  3. Structural

# Different Modelling Style

 

# Data types : Bits and Vectors in Port

```
port ( a : in std_logic; -- signal comes in to port a from outside  
      b : out std_logic; -- signal is sent out to the port b  
      c : inout std_logic; -- bidirectional port  
      x : in std_logic_vector(7 downto 0); -- 8-bit input vector  
      y : out std_logic_vector(0 downto 7) --
```

```
);  
x[7] -> MSB bit,    x[0]-> LSB bit  
y[0] -> MSB bit,    y[7]-> LSB bit
```

'U' : uninitialized      'X' : unknown

'0' : logic 0.    '1' : logic 1    'Z' : High Impedance.

**Package to be added :** `ieee.std_logic_1164.all`

# Signals Declaration and assignment

Signals are declared without direction.

Example:

```
signal s1, s2 : std_logic;
```

```
signal X, Y : std_logic_vector (31 downto 0);
```

## Signal Assignment

```
signal resetSR : std_logic_vector(3 downto 0);
```

```
resetSR <= "1111";  resetSR <= temp(2 downto 0) & '0';
```



# Other Datatypes

## SYNTHESIZABLE

integer,  
natural,  
positive,  
integer\_vector  
character,  
string

## NON SYNTHESIZABLE

real  
time

**Package to be added :** `ieee.std_logic_1164.all`

# Logical Operators

**not**

*highest precedence*

**and**

**or**

**nand**

**nor**

**xor**

***xnor***

*lowest precedence*

# ARITHMETIC:

- + addition
- - subtraction
- \* multiplication
- / division
- ABS absolute value
- MOD modulus
- REM remainder
- \*\* exponent

**Package :**

**use `ieee.NUMERIC_STD.all`;**

## Comparison Operators:

- $=$  equal to
- $\neq$  not equal to
- $<$  less than
- $>$  greater than
- $\leq$  less than or equal to
- $\geq$  greater than or equal to

# Branching Statements:

```
if condition_1 then  
    sequential statements  
elsif condition2 then  
    sequential statements  
else  
    sequential statements  
end if;
```


# Branching Statements:

```
case expression is  
    when choice =>  
        sequential statements  
    when choice =>  
        sequential statements  
end case;
```

# Circuit 1




A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 
 
# VHDL Dataflow Modelling Style

```
library ieee;  
use  
ieee.std_logic_1164.all;  
  
entity circuit_1 is  
    port (A, B: in  
          std_logic;  
          S, C: out std_logic);  
end circuit_1;
```

```
architecture dataflow of  
circuit_1 is  
    Begin  
        S <= A xor B;  
        C <= a and b;
```





# VHDL Dataflow Modelling Style

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity circuit_1 is  
    port (A, B: in std_logic;  
          S, C: out std_logic);  
end circuit_1;
```

architecture dataflow of **circuit\_1** is

Begin

```
S <= A xor B;
```

```
C <= a and b;
```

```
end dataflow;
```

# VHDL Dataflow Modelling Style

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity circuit_1 is  
  port (A, B: in std_logic;  
        S, C: out std_logic);  
end circuit_1;
```

**architecture dataflow of circuit\_1 is**

**Begin**

**S <= A xor B;**

**C <= a and b;**

**end dataflow;**

# VHDL Dataflow Modelling Style

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity circuit_1 is  
    port (A, B: in std_logic;  
          S, C: out std_logic);  
end circuit_1;
```

**architecture dataflow of circuit\_1 is**

**Begin**

**S <= A xor B;**

**C <= a and b;**


**end dataflow;**

# VHDL Behavioral Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

 architecture behavior of circuit_1 is
    Begin
        c1: process (A,B)
        Begin
            if A = '1' then
                S <= not B;
                C <= B;
            Else
                S <= B;
                C <= '0';
            end if;
        end process c1;
    end behavior;
```




# VHDL Behavioral Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

 architecture behavior of circuit_1 is
    Begin
        c1: process (A,B)
        Begin
            if A = '1' then
                S <= not B;
                C <= B;
            Else
                S <= B;
                C <= '0';
            end if;
        end process c1;
    end behavior;
```




# VHDL Behavioral Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

 architecture behavior of circuit_1 is
    Begin
        c1: process (A,B)
        Begin
            if A = '1' then
                S <= not B;
                C <= B;
            Else
                S <= B;
                C <= '0';
            end if;
        end process c1;
    end behavior;
```




# VHDL Behavioral Modelling Style


```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is
    port (A, B: in std_logic;
          S, C: out std_logic);
end circuit_1;

 architecture behavior of circuit_1 is
    Begin
        c1: process (A,B)
        Begin
            if A = '1' then
                S <= not B;
                C <= B;
            Else
                S <= B;
                C <= '0';
            end if;
        end process c1;
    end behavior;
```



# VHDL Structural Modelling Style

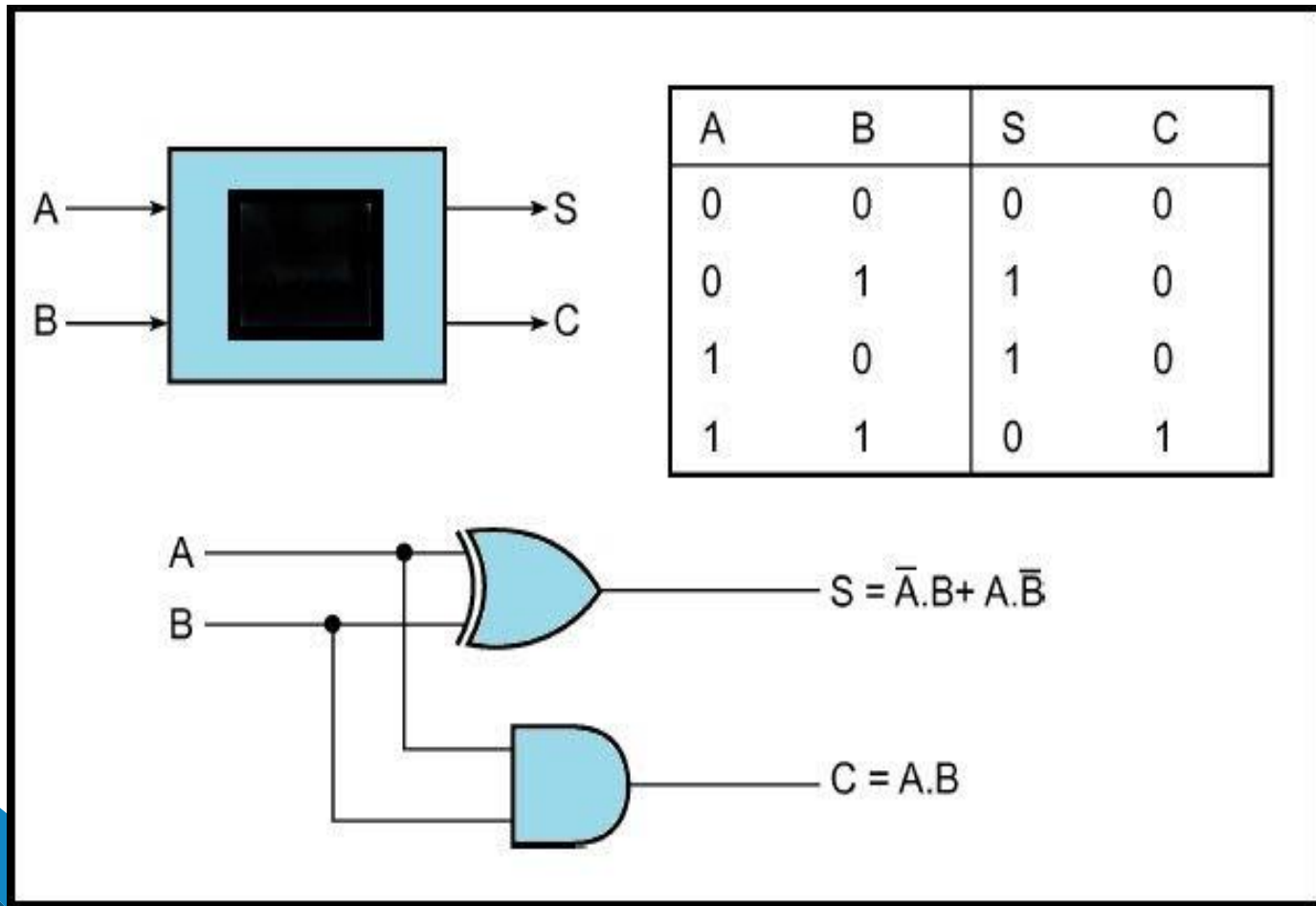



--Functionality for XOR gate in data flow modelling style

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity xor_gate is  
  port (i1, i2: in std_logic;  
        o1: out std_logic);  
end circuit_1;
```

architecture dataflow of xor\_gate is

```
  Begin  
    o1 <= i1 xor i2;  
  end dataflow;
```

--Functionality for AND gate in data flow modelling style

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity and_gate is  
    port (i3, i4: in std_logic;  
          o2: out std_logic);  
end circuit_1;  
  
architecture dataflow of and_gate is  
    Begin  
        o2 <= i3 and i4;  
    end dataflow;
```

# VHDL Structural Modelling Style

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity circuit_1 is                -- Entity declaration for circuit_1  
port (A, B: in std_logic;  
      S, C: out std_logic);  
end circuit_1;
```

```
architecture structure of circuit_1 is -- Architecture body for circuit_1  
begin
```

```
end structure;
```

# VHDL Structural Modelling Style

```
library ieee;
use ieee.std_logic_1164.all;

entity circuit_1 is                                -- Entity declaration for circuit_1
port (A, B: in std_logic;
      S, C: out std_logic);
end circuit_1;

architecture structure of circuit_1 is            -- Architecture body for circuit_1
component xor_gate                                -- xor component declaration
  port (i1, i2: in std_logic;
        o1: out std_logic);
end component;

component and_gate                                -- and component declaration
  port (i3, i4: in std_logic;
        o2: out std_logic);
end component;
```

# VHDL Structural Modelling Style

begin

```
u1: xor_gate port map (i1 => A, i2 => B, o1 => S);
```


```
u2: and_gate port map (i3 => a, i4 => b, o2 => C);
```


-- We can also use Positional Association

```
--      => u1: xor_gate port map (a, b, s);
```

```
--      => u2: and_gate port map (a, b, c);
```


end structure;

 

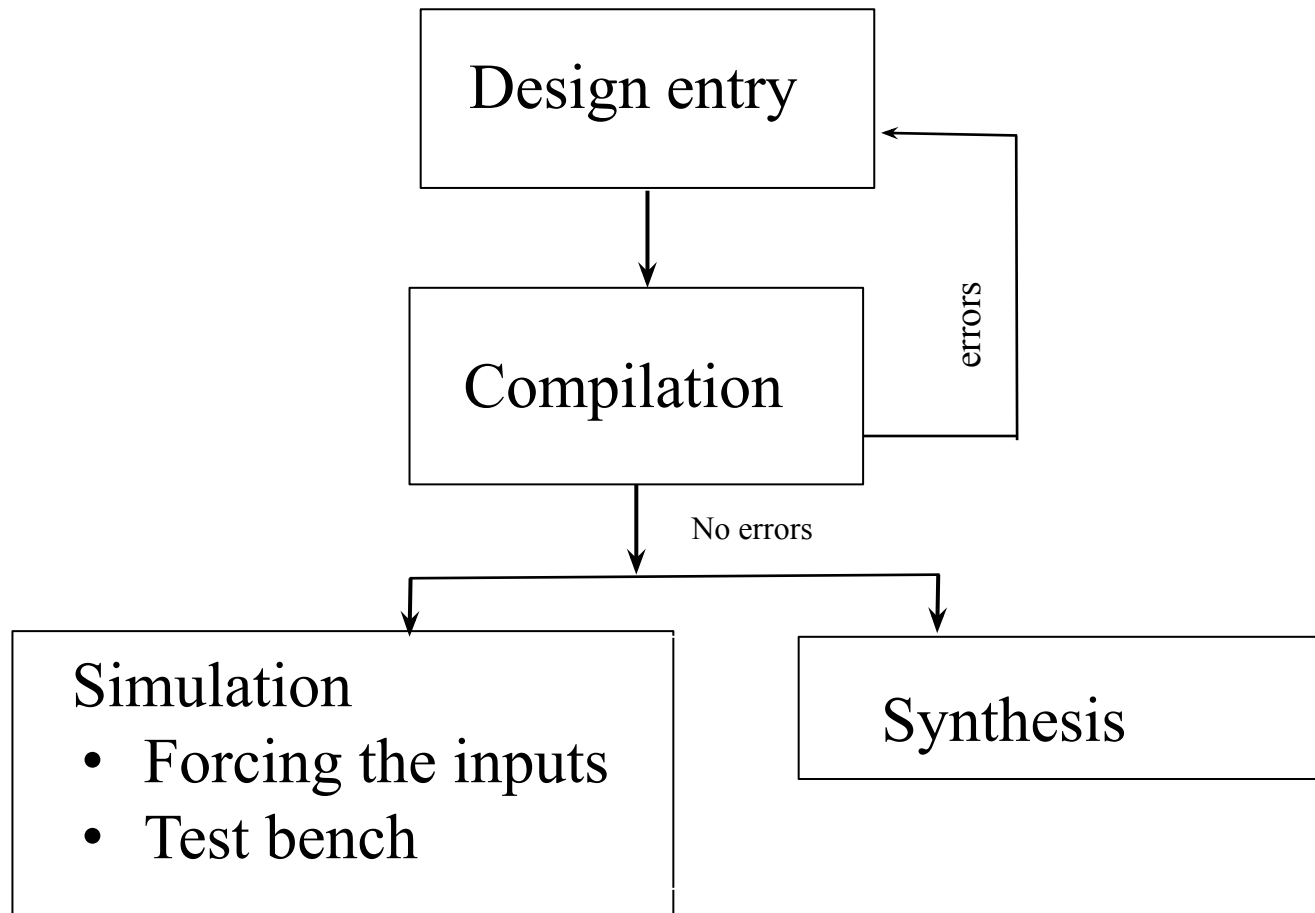
 
# Test Bench

- Used for verification of the design
- HDL code with no port list and non synthesizable constructs.
- The main objectives of Test Bench is to:
  - 1.Instantiate the design under test (DUT)
  - 2.Generate stimulus waveforms for DUT
  - 3.Generate reference outputs and compare them with the outputs of DUT
  - 4.Automatically provide a pass or fail indication




# VHDL Test Bench for Circuit 1

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY circuit_1_tb IS
END circuit_1_tb;

ARCHITECTURE circuit_1_tb OF circuit_1_tb IS

 COMPONENT circuit_1
  PORT (
    A : IN  std_logic;
    B : IN  std_logic;
    S : OUT std_logic;
    C : OUT std_logic
  );
END COMPONENT;
```



```
-- input test signals and resulting output signals from DUT to be
                        declared
```

```
signal a_tb : std_logic := '0';
signal b_tb : std_logic := '0';
signal s_tb : std_logic ;
signal c_tb : std_logic ;
```



```

BEGIN

    uut: circuit_1 PORT MAP
        (
            A => a_tb,
            B => b_tb,           -- instantate the DUT with
            S => s_tb,           -- structural modelling style
            C => c_tb
        );

    Process                       --apply the stimulus with
    Begin                       --behavioural modelling style
        a_tb <= '0';  b_tb <= '0';
        wait for 100 ps;
        a_tb <= '0';  b_tb <= '1';
        wait for 200 ps;
        a_tb<= '1';   b_tb <= '0';
        wait for 500 ps;
        a_tb <= '1';   b_tb <= '1';
        wait;
    end process;

    END circuit_1_tb ;

```



## References:

VHDL Primer by J. Bhaskar.

HDL with Digital design by Botros.



# Introduction to CPLDs

*References : <http://studytronics.weebly.com/programmable-logic-devices.html>*

# Programmable Logic Devices


An IC that contains large numbers of gates, flip-flops, etc. that can be configured by the user to perform different functions.

The internal logic gates and/or connections of PLDs can be changed/configured by a programming process.


Programming the device involves blowing those fuses along the paths to obtain particular configuration of the desired logic function.

PLDs are typically built with an array of AND gates (AND-array) and an array of OR gates (OR-array).

 
PLDs are mainly classified as (a) PROM (b) PLA (c) PAL




# PROM, PAL, PLA

 

(a) Programmable Read Only Memory (PROM)

 


 (b) Programmable Array Logic (PAL) Device



(c) Programmable Logic Array (PLA) Device

# CPLDs

 


A CPLD contains a bunch of PLD blocks whose inputs and outputs are connected together by a global interconnection matrix.

**CPLD has two levels of programmability:**

1. Each PLD block can be programmed
2. The interconnections between the PLDs can be programmed.

## Board details:

 

1. Based on Altera MAX 3000 architecture.
2. Powered and Programmed through USB.
3. 8 inputs (switches) and 8 outputs(LEDs) onboard.
4. 8 user configurable GPIOs available onboard.
5. The 8 LEDs output pins can be made available as GPIO1 pins if the DIP switches are turned OFF.
6. Onboard clock: 1Hz, 1kHz, and 10kHz available.
7. Provision for connecting external clock signal.

## INPUT AND OUTPUT PINS DETAILS OF MAX 3000A

Inputs	Pin No.
SW1	4
SW2	5
SW3	6
SW4	8
SW5	9
SW6	11
SW7	12
SW8	14

Outputs	Pin No.
LED1	24
LED 2	25
LED 3	26
LED 4	27
LED 5	28
LED 6	29
LED 7	31
LED 8	33



# Configuring Helium Board using JTAG

1. Open terminal -> jtag
2. cable ft2232 vid=0x0403 pid=0x6010
3. detect
- 4.svf “file path.svf”